 




Chapter3: Multiplexer, Latch, Buffer

Asst.Prof.Dr.Supakit Nootyaskool



Objective

- Explain the concept of multiplexer and de-multiplexer circuit in the data communication system @ 26 Telecom
- Understand the different between the latch circuit and buffer circuit.
- Explain the truth table of Set-Reset flipflop also know the circuit.

Topic


- Multiplexer circuit
- Demultiplexer circuit
- Latch circuit
- Buffer circuit
- Set-Reset Flipflop

MULTIPLEXER CIRCUIT

Student will able to explain the multiplexer circuit.

Student realizes the important of the multiplexer circuit in the communication system.

Selector switch

 



ဖွဲ့စည်းပုံအား Internet မှ ရှာဖွေရပါသည်။

ပေါ့လွယ်စွာ အသုံးပြုနိုင်သော, Microwave



A selector switch is a mechanical switch used to select between different signal channels. Selector switches are commonly found in electrical machines, radios, and even in vehicles.

Switch -> Multiplexer (MUX)

  

LazGlobal CD74HC4067 16-Channel Analog Digital Multiplexer Breakout Board Module For Arduino

★★★★★ 1 คะแนน



แบรนด์: No Brand

฿36.00


฿50.00 -28%

โปรโมชั่น


จำนวน

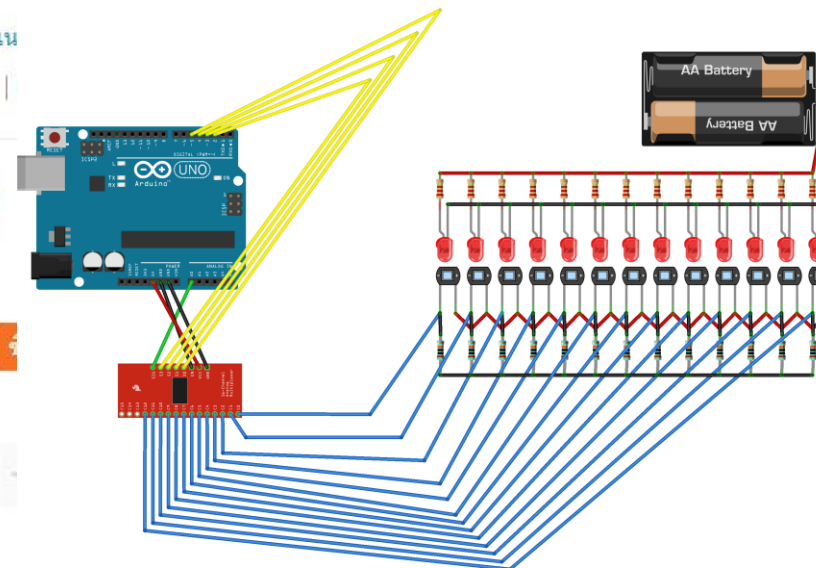 


Compare between No MUX and MUX

 

What is circuit inside MUX and DEMUX

 


 ↓ select อาจจะมี/ไม่มี
(ใช้กับ synchronize เวลาทำงาน
ถ้า มีสัญญาณ → channel ไปแล้ว)




วิชาอิเล็กทรอนิกส์
MUX / DEMUX

Multiplexer circuit

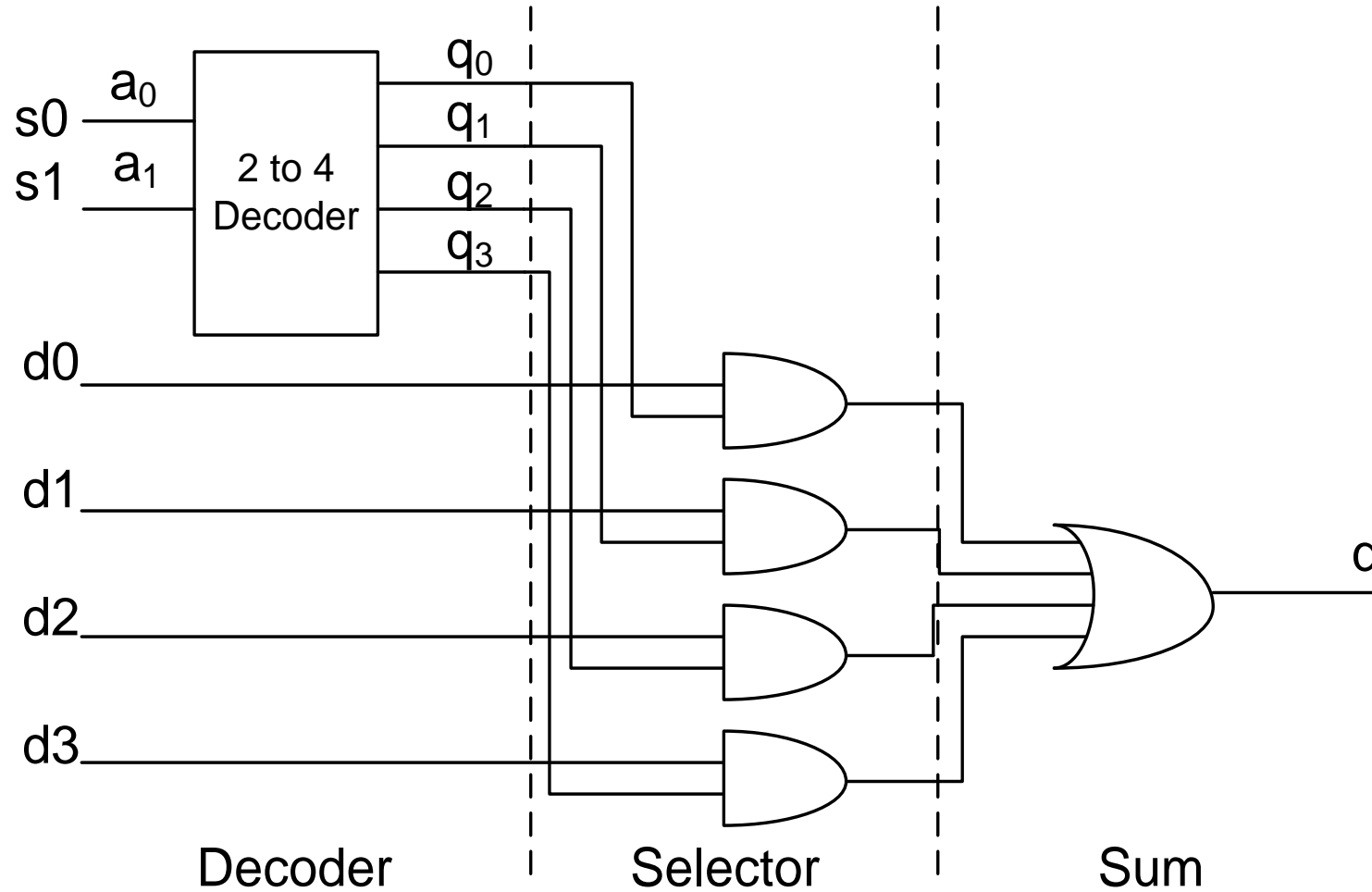

Multiplexer circuit

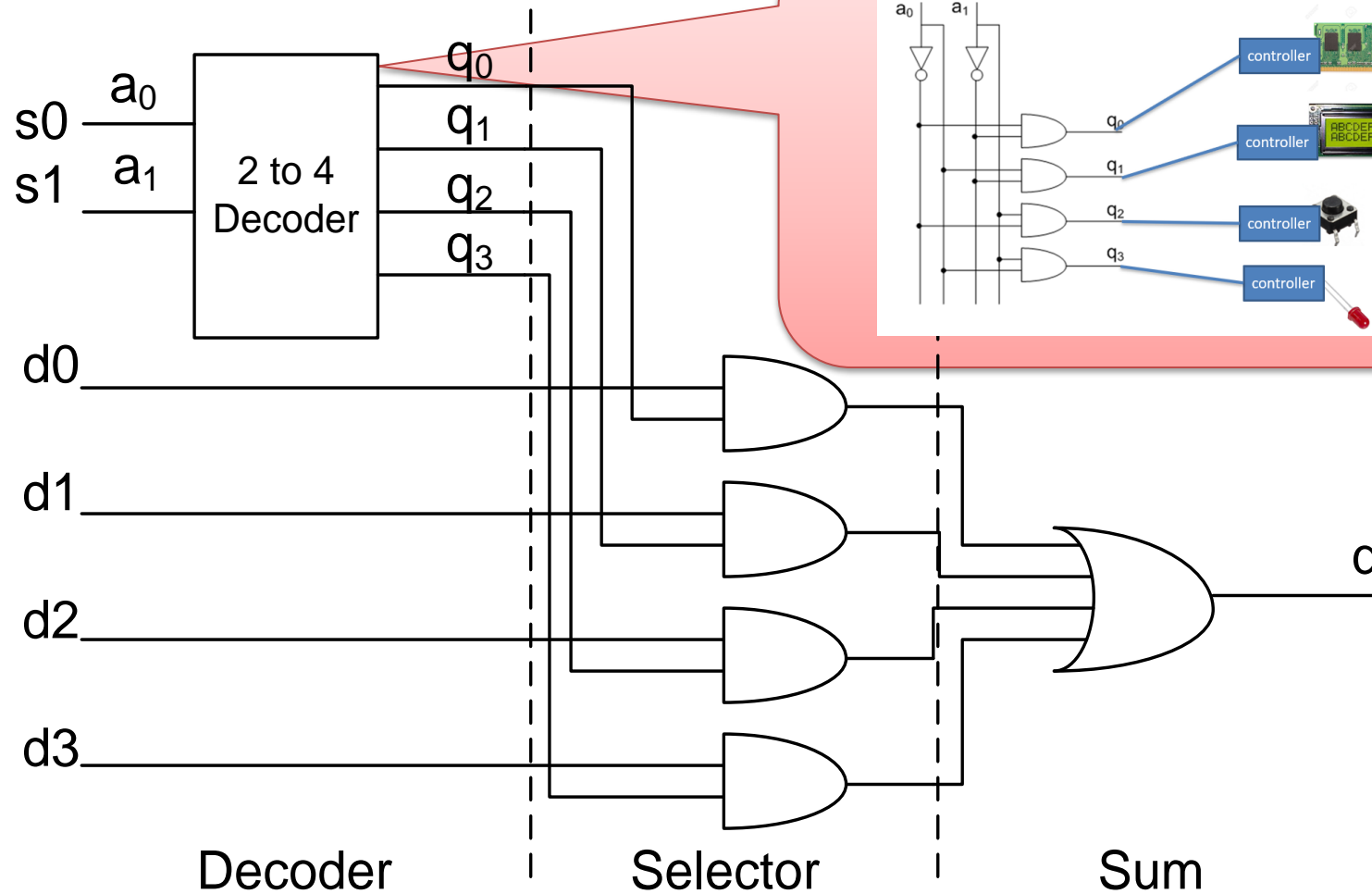


DEMULTIPLEXER CIRCUIT


Student will be able to understand the data switching in the multiplexer through the demultiplexer circuit .

De-multiplexer circuit


ସୂଚୀ 1 ଉପରେ ନିର୍ଦ୍ଧାରିତ

 

MUX + DEMUX

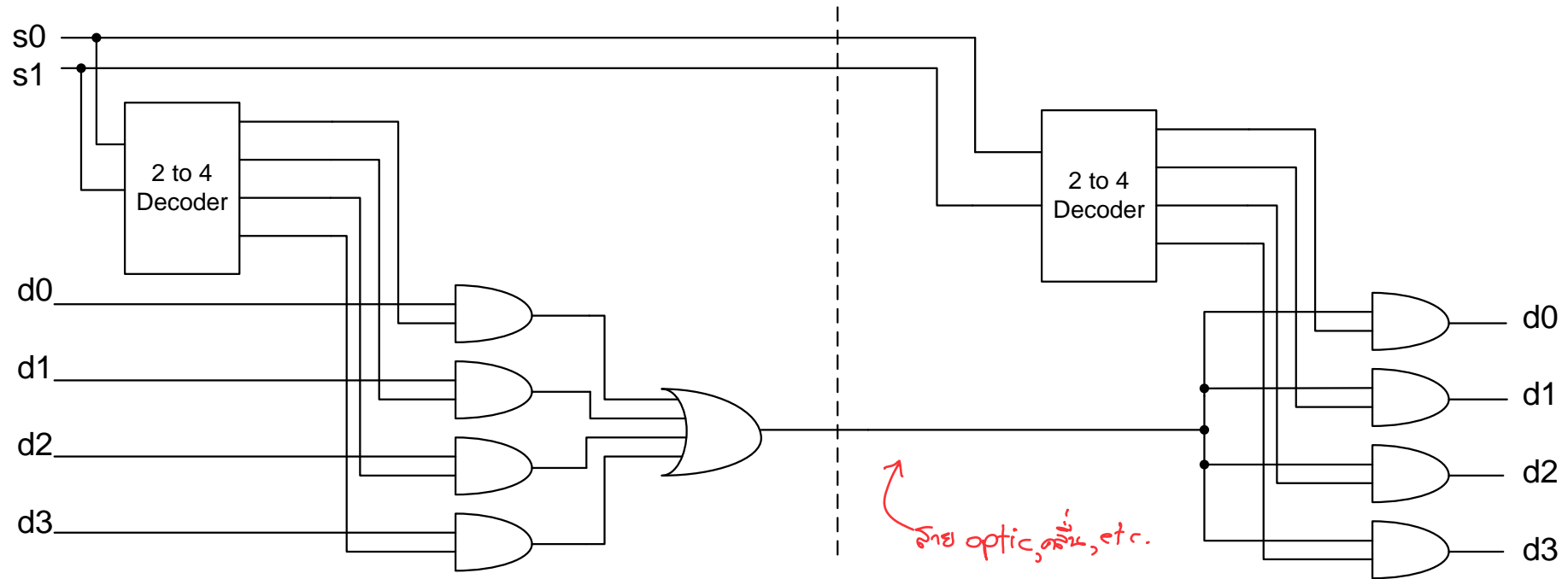

Example devices use MUX/DMUX

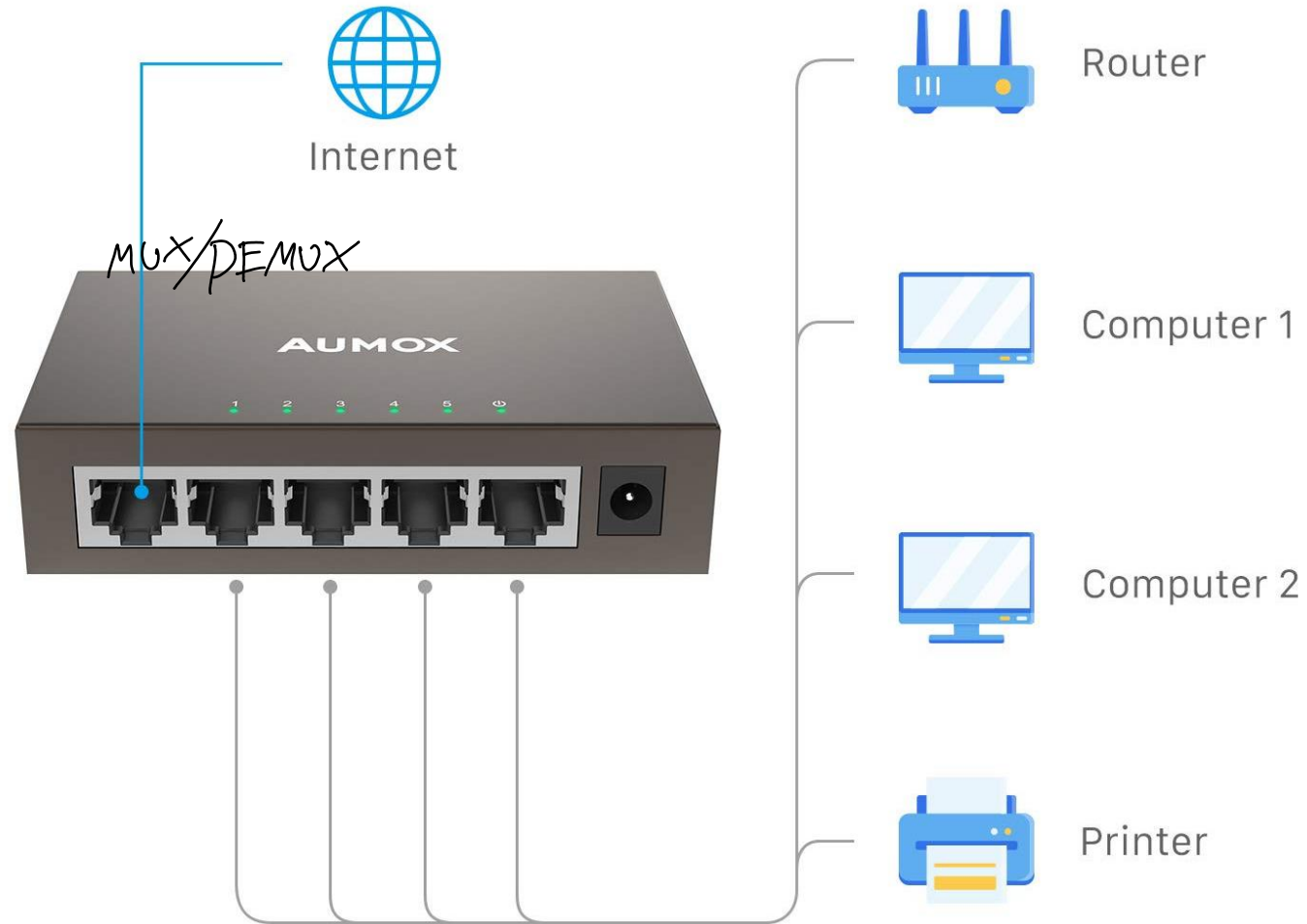

trai-state gate

TRISTATE GATE


Student will understand the role of tristate gate in the switching circuit.

Student will able to explain the state of high implement in the digital system.

Tristate gate


- Three possible logic levels:
 - Logic high (H)
 - Logic low (0V)
 - High impedance (Z) ค่าความต้านทาน > 1MΩ
- High impedance (Z) occurs when the output behaves like an open circuit (disconnecting).
- High impedance typically exceeding 1MΩ. like open circuit.

↳ ง่ายไปมาก

 

Enable	Input	Output
0	0	Hi-Z
0	1	Hi-Z
1	0	1
1	1	0

 แต่ถ้า Enable เป็น 0 จะ active ที่ 0 หรือ 1



Tristate gate datasheet and package

3CE32231 - APRIL 1999 - REVISED OCTOBER 2014

SN74LVC1G125 Single Bus Buffer Gate With 3-State Output

1 Features

- Available in the Ultra Small 0.64-mm² Package (DPW) With 0.5-mm Pitch
- Supports 5-V V_{CC} Operation
- Inputs Accept Voltages to 5.5 V
- Provides Down Translation to V_{CC}
- Max t_{pd} of 3.7 ns at 3.3 V
- Low Power Consumption, 10- μ A Max I_{CC}
- ± 24 -mA Output Drive at 3.3 V
- I_{off} Supports Live Insertion, Partial-Power-Down Mode, and Back-Drive Protection
- Latch-Up Performance Exceeds 100 mA Per JESD 78, Class II
- ESD Protection Exceeds JESD 22
 - 2000-V Human-Body Model (A114-A)
 - 200-V Machine Model (A115-A)
 - 1000-V Charged-Device Model (C101)

2 Applications

- Cable Modem Termination System
- High-Speed Data Acquisition and Generation
- Military: Radar and Sonar
- Motor Control: High-Voltage
- Power Line Communication Modem
- SSD: Internal or External
- Video Broadcasting and Infrastructure: Scalable Platform
- Video Broadcasting: IP-Based Multi-Format Transcoder
- Video Communications System

3 Description

This bus buffer gate is designed for 1.65-V to 5.5-V V_{CC} operation.

The SN74LVC1G125 device is a single line driver with a 3-state output. The output is disabled when the output-enable (OE) input is high.

The CMOS device has high output drive while maintaining low static power dissipation over a broad V_{CC} operating range.



The SN74LVC1G125 device is available in a variety of packages including the ultra-small DPW package with a body size of 0.8 mm \times 0.8 mm.

Device Information⁽¹⁾

DEVICE NAME	PACKAGE	BODY SIZE (NOM)
SN74LVC1G125	SOT-23 (5)	2.90 mm \times 1.60 mm
	SC70 (5)	2.00 mm \times 1.25 mm
	SON (6)	1.45 mm \times 1.00 mm
	DSBGA (5)	1.40 mm \times 0.90 mm
	X2SON (4)	0.80 mm \times 0.80 mm

(1) For all available packages, see the orderable addendum at the end of the data sheet.

4 Simplified Schematic

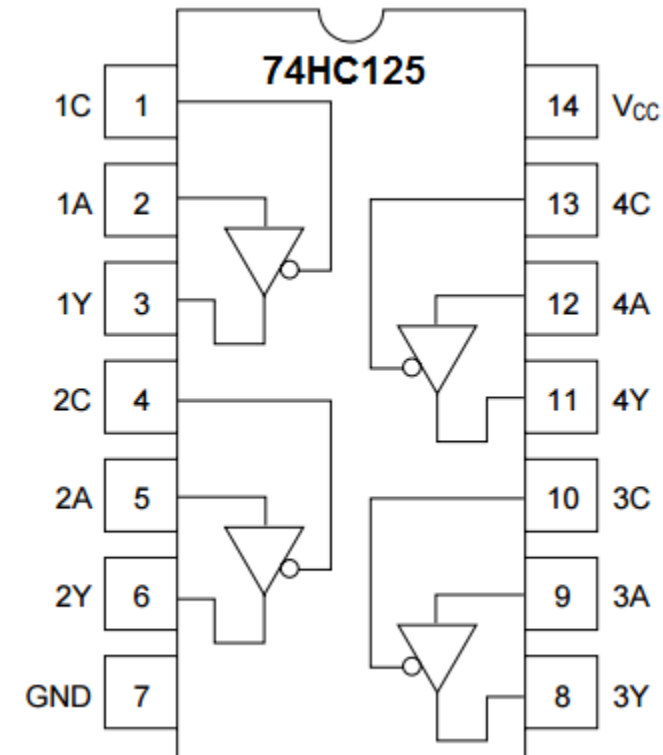 

LATCH AND BUFFER

Student will able to explain the different between the latch and buffer.

Latch vs Buffer


ကလေးအသံထွက်ပေးရန် Buffer ကို

မိမိအသံထွက်

- **Latch:** A latch is used in digital circuits to hold data. The data in the latch remains unchanged until a clearing or enabling signal is sent, which triggers the data to change. Essentially, the latch's primary function is to store memory.
- **Buffer:** A buffer operates with both analog and digital signals. Unlike latches, buffers are not just used for holding memory. They serve additional purposes, such as increasing output power or altering output impedance.


အသံထွက်အား

Latch/buffer concept

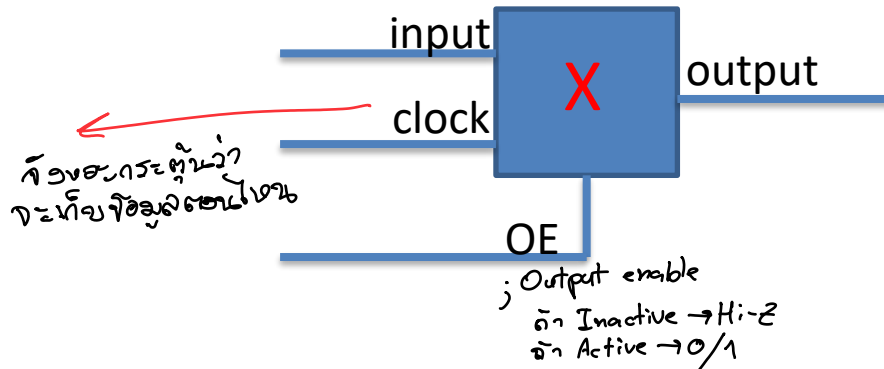

Latch circuit functions

 
- Holds data from the input signals
- Controls data retention using a clock or enable pin
- Includes an output enable pin that control on/off state of the output signal



Buffer circuit functions


- No hold data
- Pass through data by amplifying the signal
- Some buffer has an enable pin that control on/off state of the output signal

Work of the buffer circuit

 


“Z” means a high-impedance state similar to the open circuit.


Work of the buffer circuit

 


Work of the buffer circuit

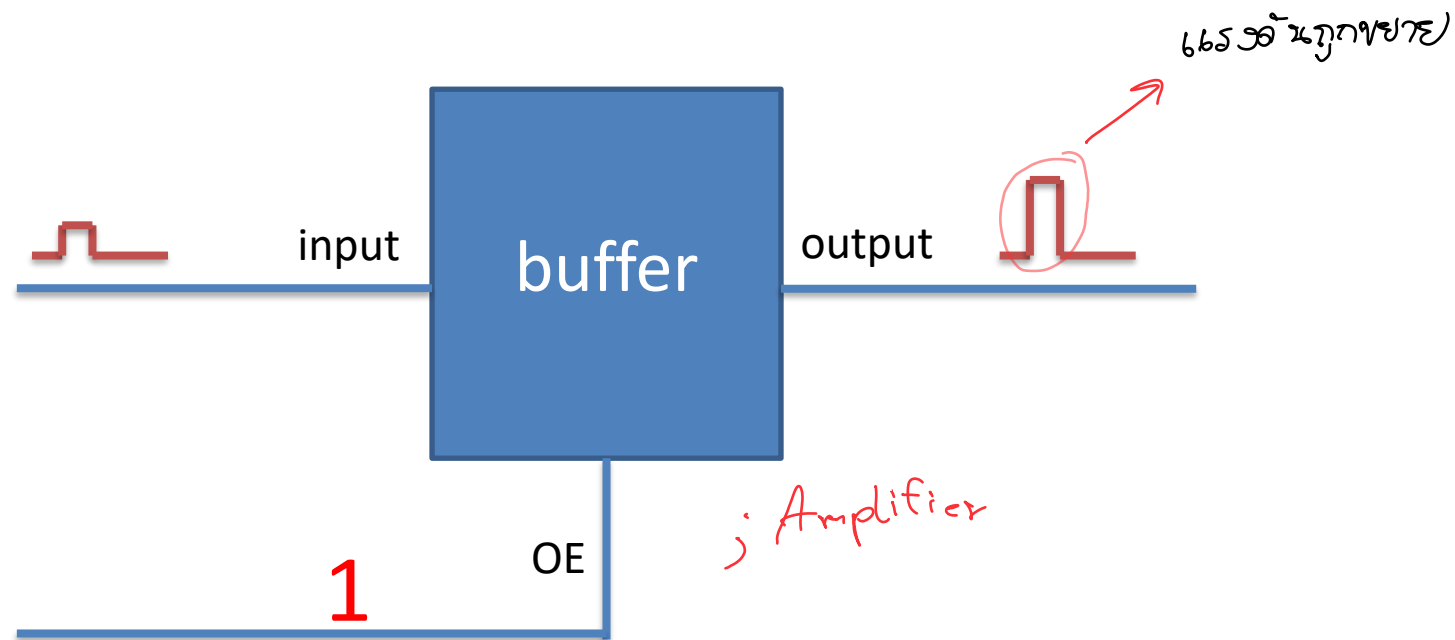


Work of the latch circuit

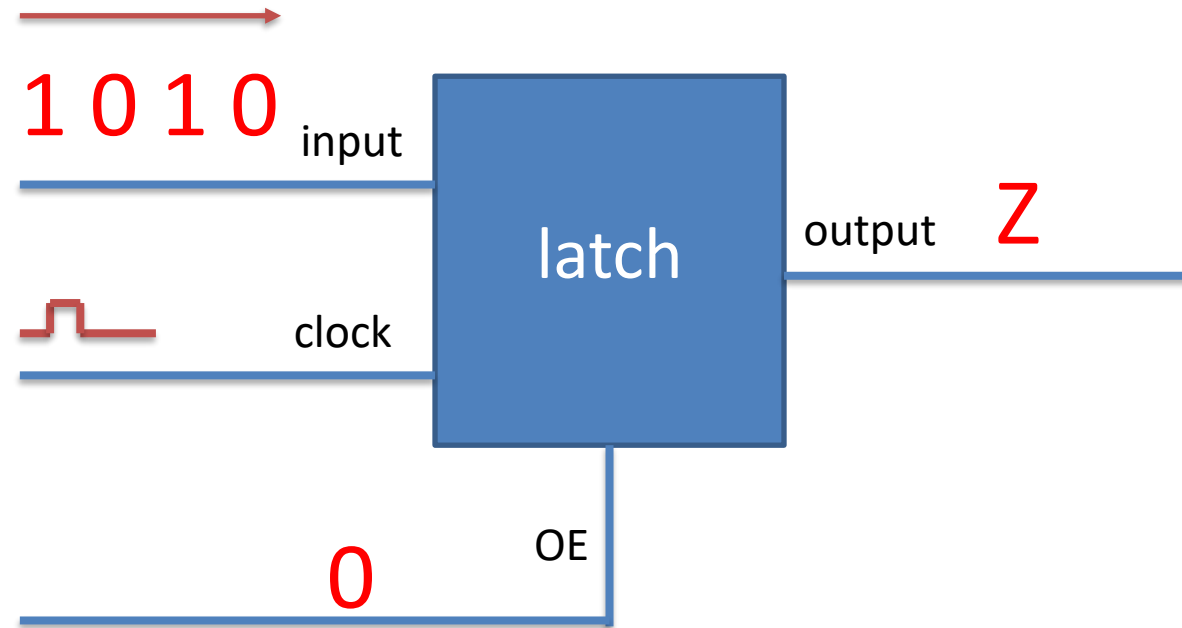


Work of the latch circuit

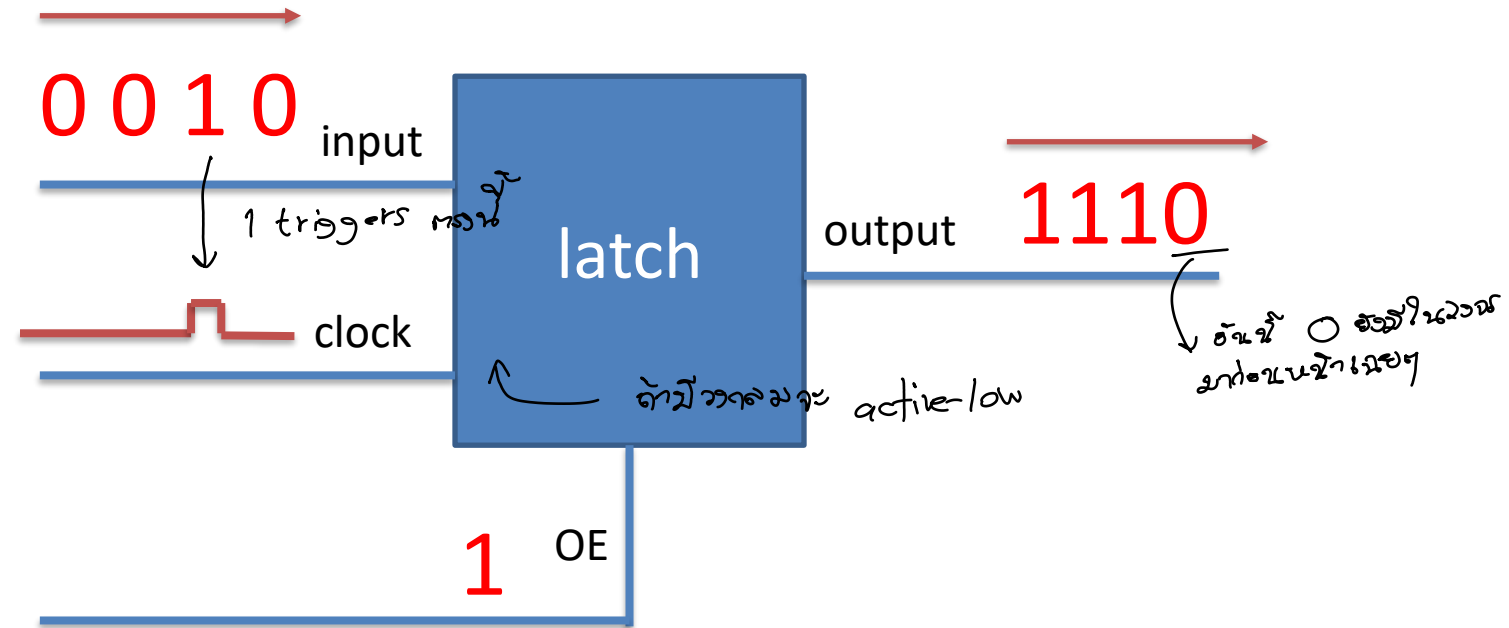



Work of the latch circuit

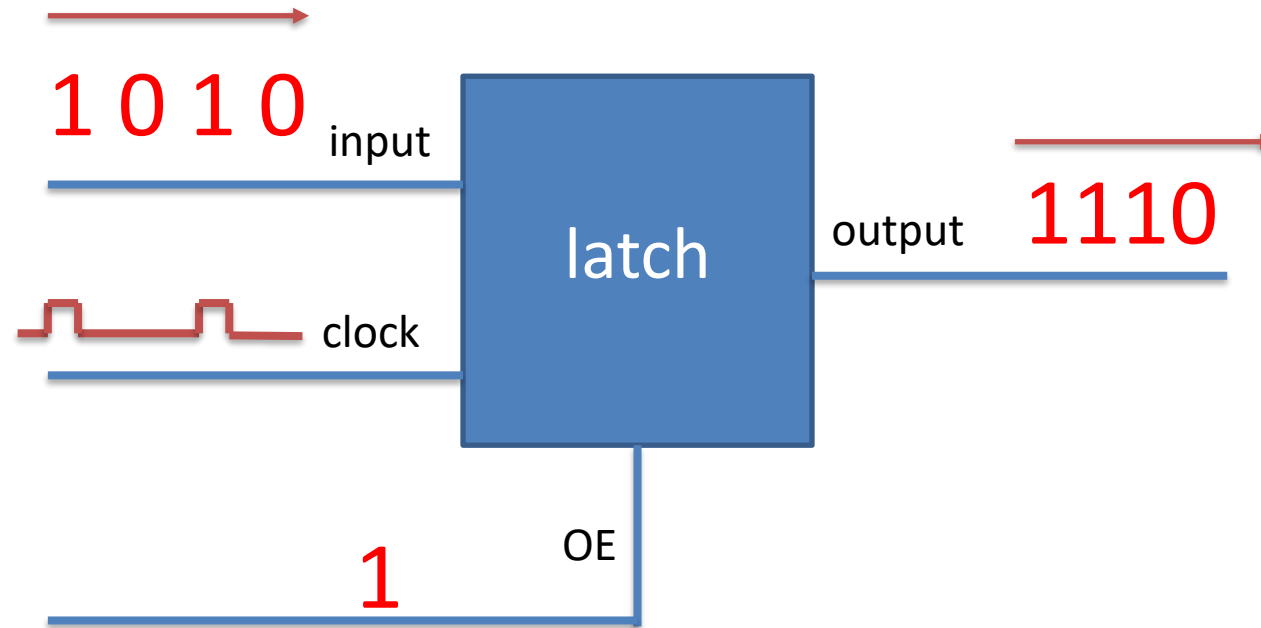

Latch/buffer in the computer

 

Last Minute
ENGINEERS.com

  


รวม Flip-Flop

↳ Latch → ใช้ในคอมพิวเตอร์

SET-RESET FLIP-FLOP


SR Flip-Flop truth table

 

S	R	Q	State
0	0	Previous state	No change
0	1	0	Reset
1	0	1	Set
1	1	?	Forbidden

→ 1 ได้ ๖ ค่า

SR Flip-flop analysis

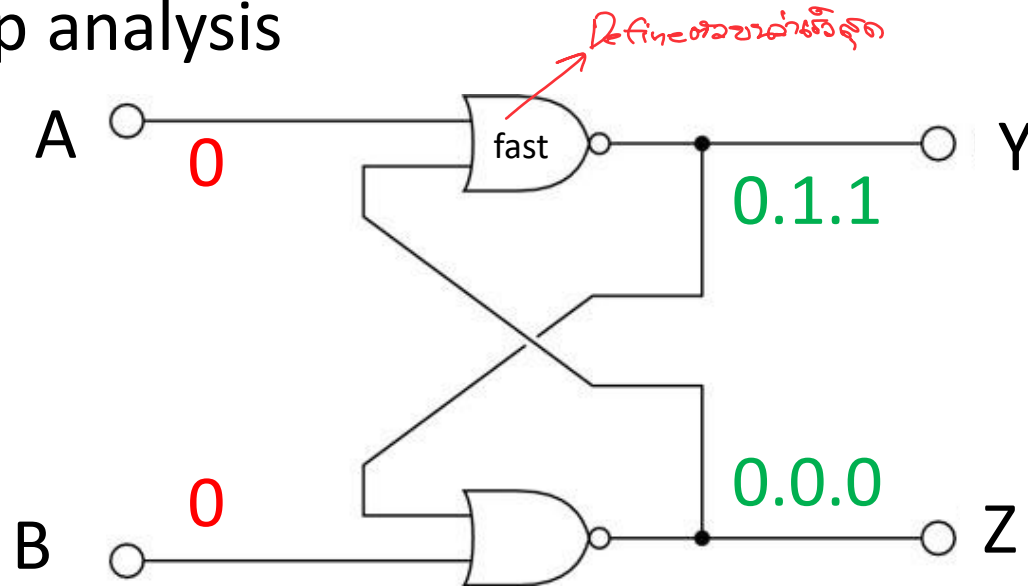


NOR
00 1
01 0
10 0
11 0

Step1

A	B	Y	Z
0	0	1	0
0	1		
0	0		
1	0		
0	0		
0	1		

SR Flip-flop analysis

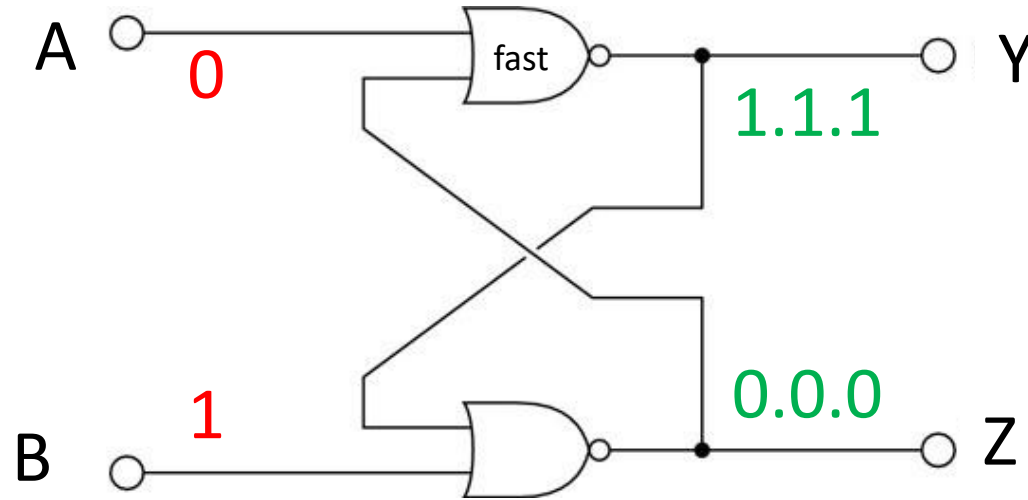


NOR
00 1
01 0
10 0
11 0

Step2

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0		
1	0		
0	0		
0	1		

SR Flip-flop analysis

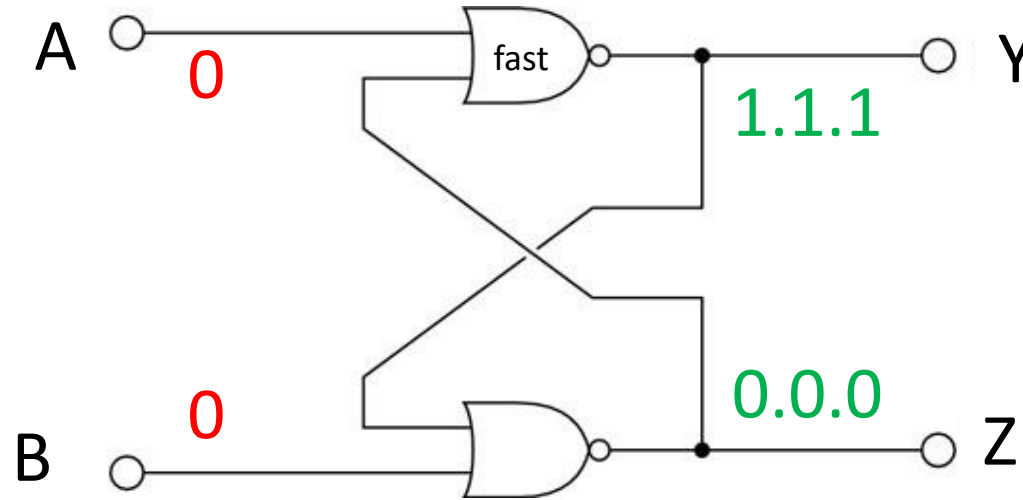


NOR
00 1
01 0
10 0
11 0

Step3

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0		
0	0		
0	1		

SR Flip-flop analysis

 


NOR
00 1
01 0
10 0
11 0

Step4

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0	0	1
0	0		
0	1		

SR Flip-flop analysis

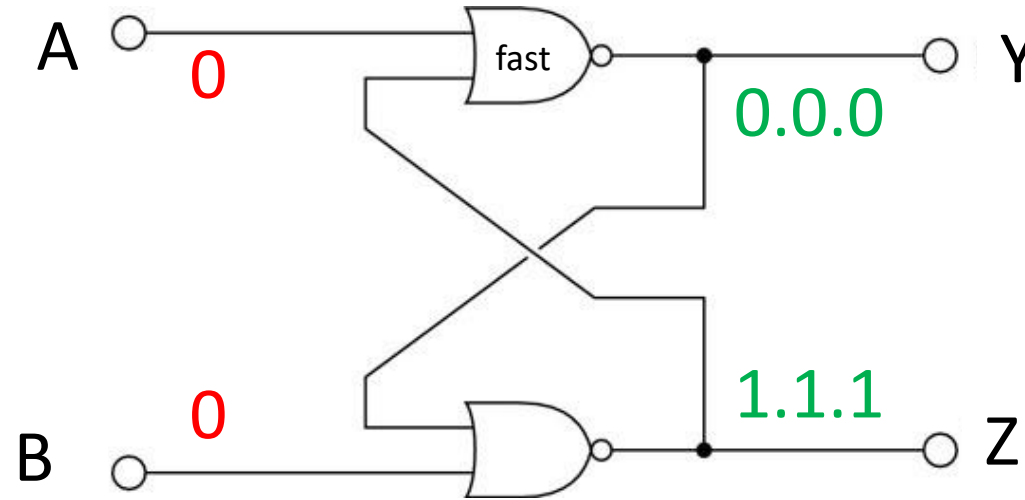


NOR
00 1
01 0
10 0
11 0

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
0	1		



SR Flip-flop analysis

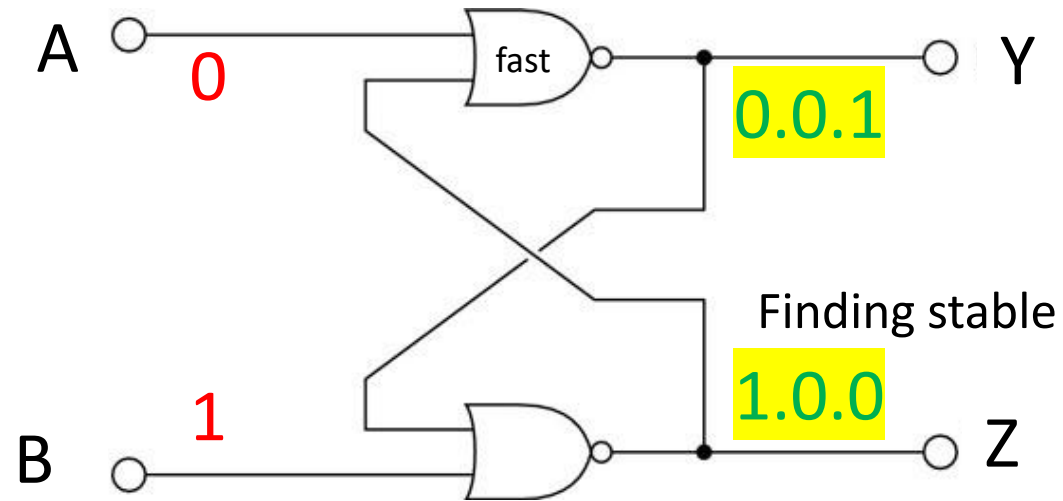


NOR
00 1
01 0
10 0
11 0

A	B	Y	Z
0	0	1	0
0	1	1	0
0	0	1	0
1	0	0	1
0	0	0	1
0	1	1	0

Step6


Truth table of SET/RESET – Flip Flop

 


NOR
00 1
01 0
10 0
11 0

Reset	Set	Q	Q'	
0	0	1	0	
0	1	1	0	
0	0	1	0	No change
1	0	0	1	
0	0	0	1	No change
0	1	1	0	

Activity 3.1 Build the SR flipflop on ThinkerCAD

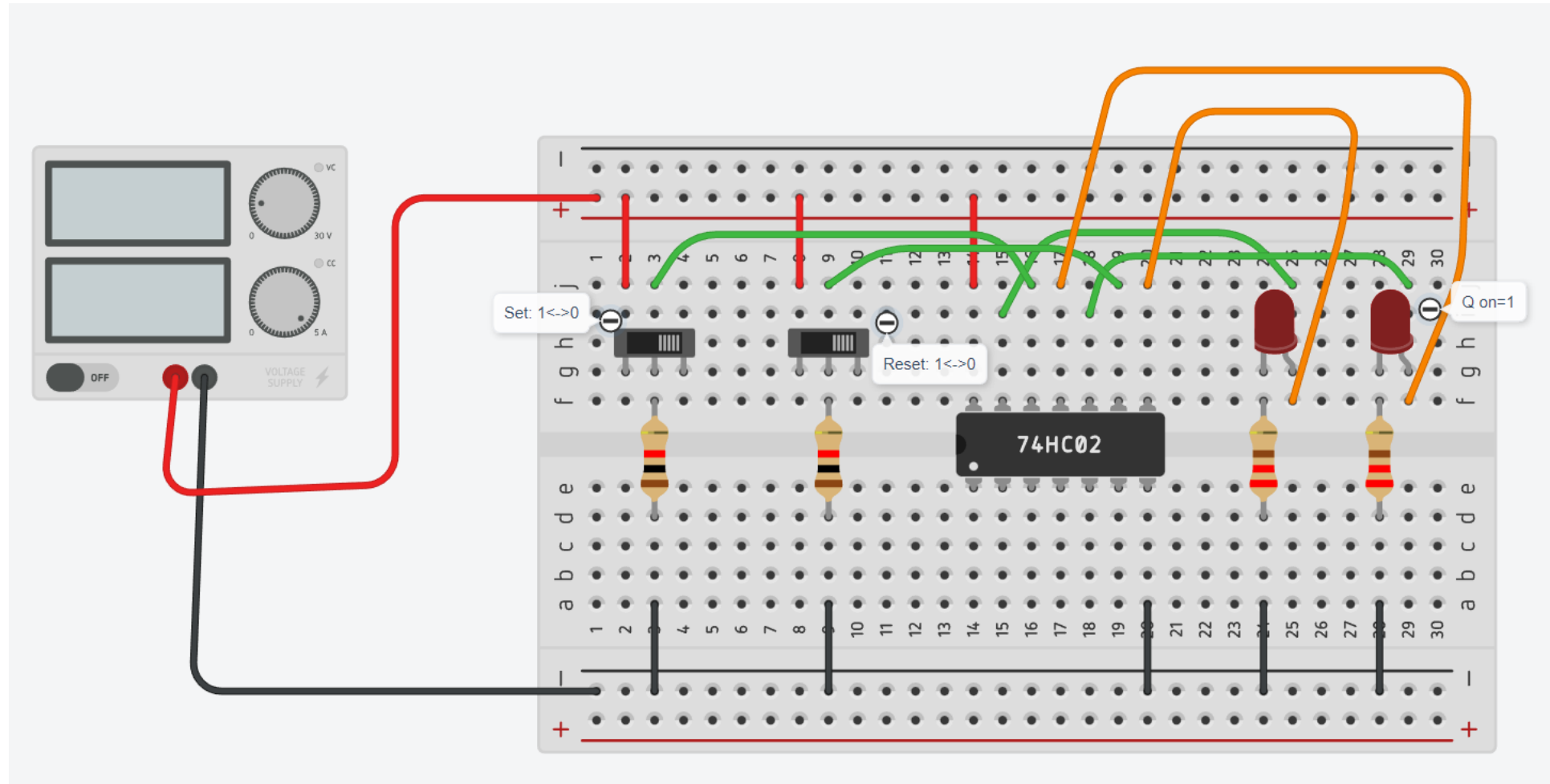

 Activity 3.2 Build the SR flipflop with clock on ThinkerCAD



Reference